



# 计算机科学基础 C



北京<sup>1</sup>大学



# Verilog 设计技巧与实践



清华大学<sup>2</sup>



# Verilog 设计技巧与实践

- ✱ 阻塞赋值与非阻塞赋值
- ✱ 同步设计及异域信号的处理
- ✱ 再谈有限状态机
- ✱ 块思维
- ✱ 代码规范





# 阻塞赋值与非阻塞赋值





# 阻塞赋值与非阻塞赋值

## ※什么叫阻塞赋值？

- ☞ 见到阻塞赋值立刻赋值，赋值完成后，才可执行下一条语句。
- ☞ 用 “=” 表示


## ※什么叫非阻塞赋值？

- ☞ 等待过程块中所有非阻塞赋值统一节拍，在过程块最后时刻赋值。
- ☞ 用 “<=” 表示









# 如何区分

 

阻塞赋值：  
电路输出实时根据输入变化而变化

  

非阻塞赋值：  
赋值先被挂起，等待其他赋值完成后，  
一同赋值

  

何时使用

时序电路


组合电路



清华大学

# 时序电路

基于触发器的  
数字延迟链

 

使用阻塞赋值和非阻塞赋值实现，电路综合结果？

```
module nonblocking(in, clk, out);  
    input in, clk;  
    output out;  
    reg q1, q2, out;  
    always @ (posedge clk)  
    begin  
        q1 <- in;  
        q2 <= q1;  
        out <= q2;  
    end  
endmodule
```

```
module blocking(in, clk, out);  
    input in, clk;  
    output out;  
    reg q1, q2, out;  
    always @ (posedge clk)  
    begin  
        q1 = in;  
        q2 = q1;  
        out = q2;  
    end  
endmodule
```








# 时序电路


```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

在每个时钟上升沿q1,q2,out  
分别接收到前一级in,q1,q2的值

 

```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

 在每个时钟上升沿q1=in,q2=q1=in,  
out=q2=q1=in, 中间电路别优化掉



阻塞赋值在时序链上没能起到延时传输的目的，所以说  
在时序电路中，永远使用非阻塞赋值 <=






# 组合电路

## Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x   c;	0	1	0	0	0

```
always @ (a or b or c)
begin
    x = a & b;
    y = x | c;
end
```

 

## Nonblocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x <= a & b;	0	1	0	1	1
y <= x   c;	0	1	0	1	1
Assignment completion	0	1	0	0	1

## Deferred

```
always @ (a or b or c)
begin
    x <= a & b;
    y <= x | c;
end
```

非阻塞赋值在组合电路中不可实时影响电路输出值，所以在组合电路中，永远使用阻塞赋值 =






# 阻塞赋值与非阻塞赋值

※ 时序电路一律使用非阻塞赋值  $\leftarrow$

※ 组合电路一律使用阻塞赋值  $=$



## 实例：LED灯开关

 

如何实现？




# 同步设计及异地信号处理





# 同步设计

 


- 我们要求整个电路共用一个时钟；
- 要求时钟应该直接接入时钟输入端；
- 对于组合电路模块，只关心触发沿到来前一刻，组合电路的输出值；
- 时钟周期应大于每个组合电路块的延时；

所有电路 = 组合电路模块 + 时序电路结点


 
# 同步电路


```
module onoff(button,light);  
  input button;  
  output light;  
  reg light;  
  always @ (posedge button)  
  begin  
    light <= ~light;  
  end  
endmodule
```



# 同步电路

```
module onoff(clk,button,light);  
    input clk,button;  
    output light;  
    reg light;  
    always @ (posedge  
begin  
    if (button) light  
end  
endmodule
```

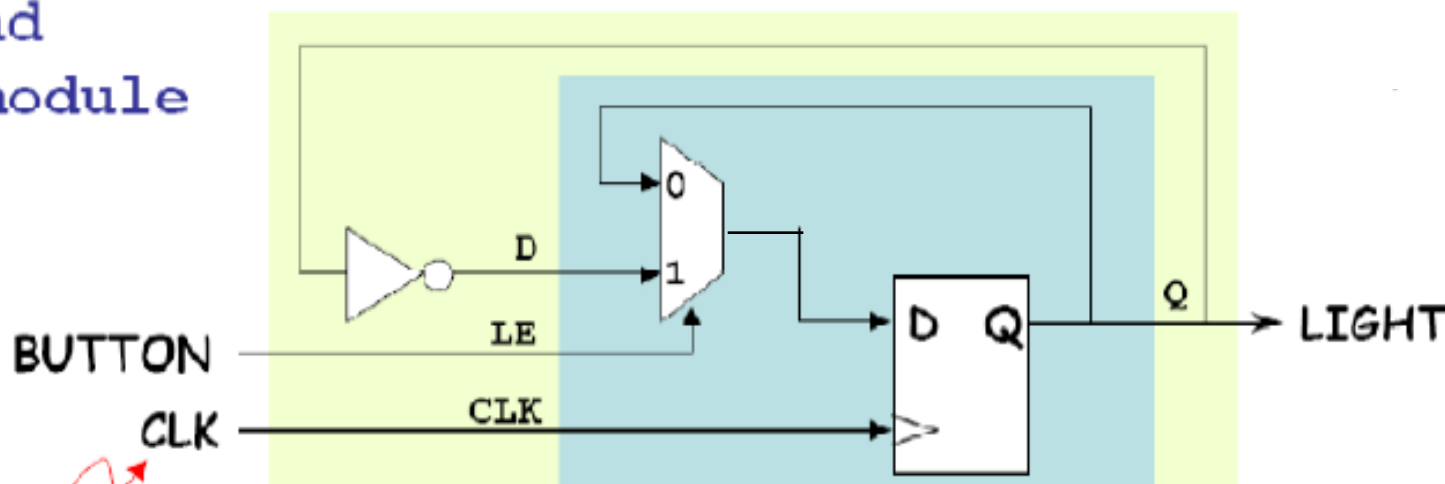- 1、如何保证Button单脉冲？
- 2、如何保证单脉冲Button在触发沿上稳定，在触发的沿激励下同步跳变？



全局单时钟

引入使能信号，控制电路








# 异域信号进入的三种情况




如何保证这个异域信号满足建立时间和保持时间？


## 异域信号进入同步电路

 

第一个clk沿没抓到信号变化，第二个clk沿抓到信号变化。

 

第一个clk沿就抓到信号变化了。

 

抓到信号变化后，输出不稳定，即亚稳态。

哪个会对电路产生影像？







# 异域信号的处理

在一个电路中，同时发生以上两种情况，则电路将出现错误！

异域信号进门时，先用同步时钟打一拍，则可防止I、II的发生。

  

针对第三种情况，亚稳态信号如何处理？






# 如何消除亚稳态

要想消除电路的亚稳态，是不可能的。

使用高增益的器件，可以很快恢复信号的稳定输出。

解决方法：用时间成本逐级减小亚稳态产生概率。

 


入口处加几级同步触发器合适？



# 如何消除亚稳态

异步信号入门，用同步时钟打两拍。

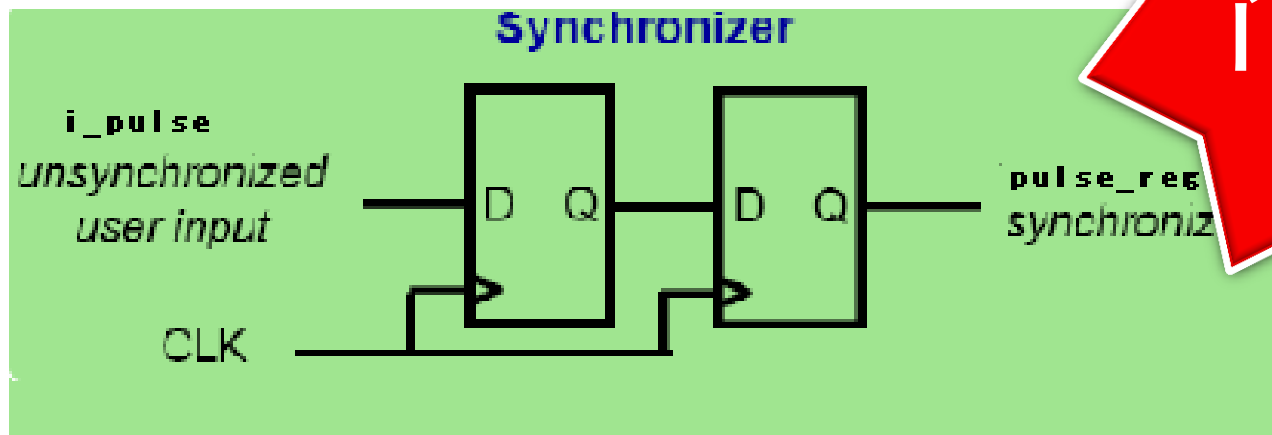

门 规

```
pulse_reg[0] <= i_pulse;
```

```
pulse_reg[1] <= pulse_reg[0];
```






# 再谈有限状态机





# 再谈有限状态机


什么是有限状态机？

 


# 再谈有限状态机

两种有限状态机:

- Moore FSM:

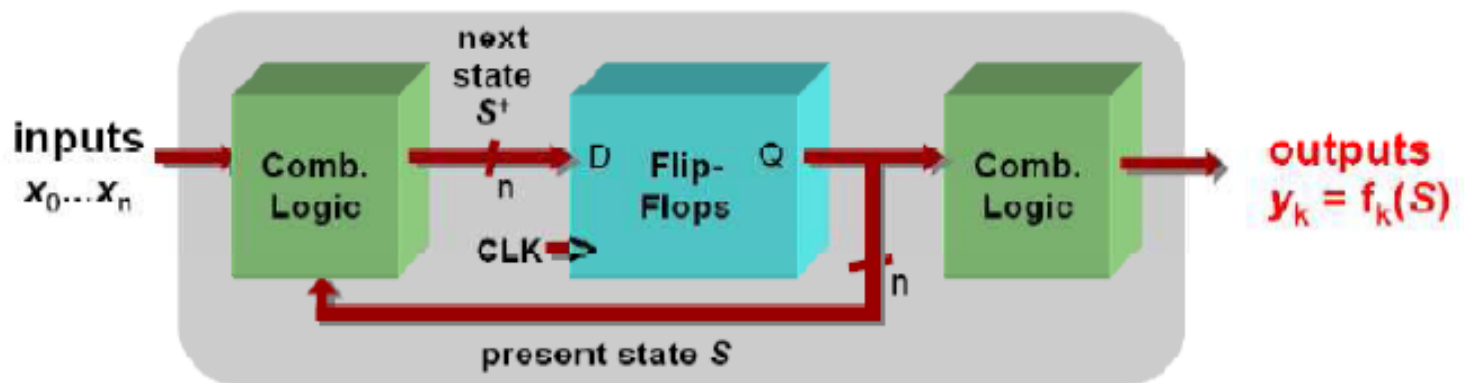

- Mealy FSM:

 






# 再谈有限状态机

## 点灯问题

 



# 再谈有限状态机

## Level To Pulse Converter:


当按键按下，产生一个周期高脉冲。

应用：

A、按键开关

B、counter的使能信号



.....

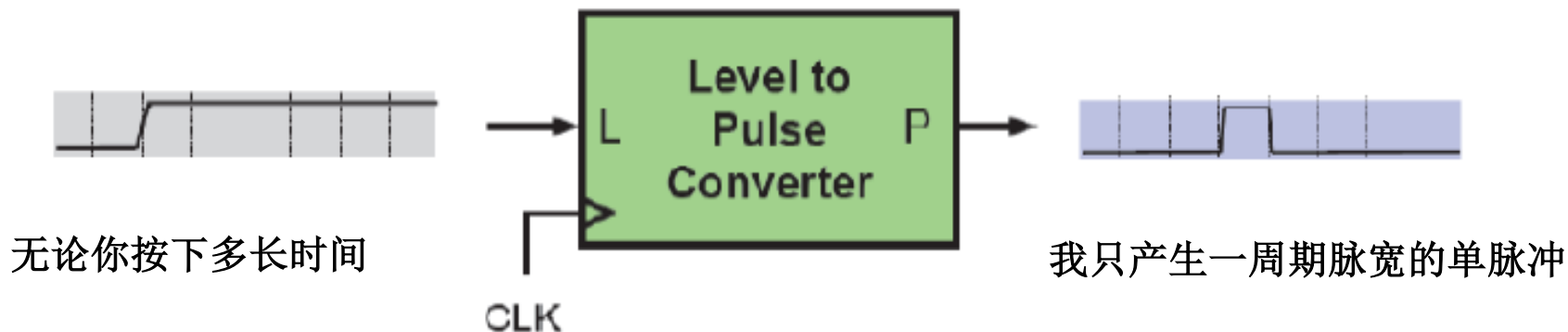



# 再谈有限状态机

电路设计:

  




# 再谈有限状态机

电路实现: :

状态转移图  $\longrightarrow$  真值表

 

Current State		In	Next State		Out
$S_1$	$S_0$	$L$	$S_1^+$	$S_0^+$	$P$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0


真值表  $\longrightarrow$  卡诺图

for  $S_1^+$ :

$L$	$S_1 S_0$	00	01	11	10
0		0	0	0	X
1		0	1	1	X

for  $S_0^+$ :

$L$	$S_1 S_0$	00	01	11	10
0		0	0	0	X
1		1	1	1	X

 


for  $P$ :

$S_0$	$S_1$	0	1
0		0	X
1		1	0




# 再谈有限状态机

电路实现:

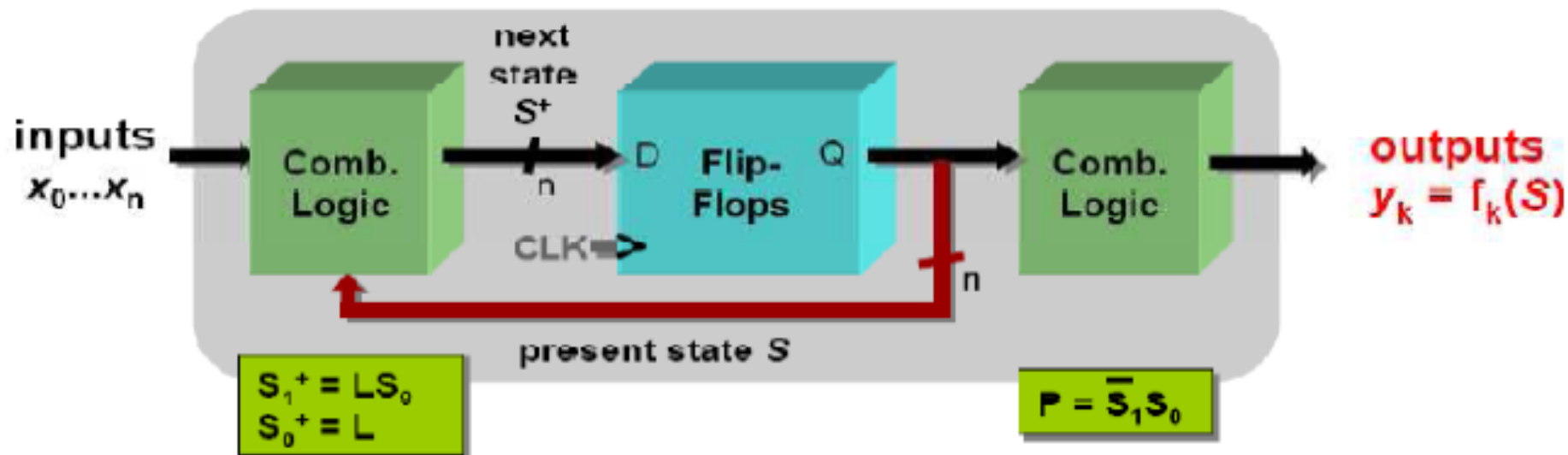

用moore状态机实现level to pulse电路:

 


# 再谈有限状态机

代码实现:

```
module pulse_FSM (Clock, Resetn, i_pulse, o_pulse);
    input Clock, Resetn, i_pulse;
    output reg o_pulse;
    reg [1:0] cs, ns; // present and next state variable
    reg [1:0] pulse_reg;
    parameter S0 = 0, S1 = 1, S2 = 2;
```
 
```
always @(posedge Clock)
begin
    pulse_reg[1] <= pulse_reg[0];
    pulse_reg[0] <= i_pulse;
    if (Resetn == 1'b0) // synchronous clear
        cs <= S0;
    else
        cs <= ns;
end
```



```
always @(cs, pulse_reg[1])
begin: state_table
    case (cs)
        S0:    if (pulse_reg[1]) begin
                    ns = S1;
                    o_pulse = 1'b1 end
                else begin
                    ns = S0;
                    o_pulse = 1'b0; end
        S1:    if (pulse_reg[1]) begin
                    ns = S2;
                    o_pulse = 1'b0 end
                else begin
                    ns = S0;
                    o_pulse = 1'b0;
        S2:    iif (pulse_reg[1]) begin
                    ns = S2;
                    o_pulse = 1'b0 end
                else begin
                    ns = S0;
                    o_pulse = 1'b0; end
        default: ns = 2'bxx;
    endcase
end // state_table
endmodule
```








# 再谈有限状态机

电路实现：：


当前状态的输出由当前状态和输入共同决定的状态机成为mealy状态机

 







# 再谈有限状态机

 

Pres. State	In	Next State	Out
$S$	$L$	$S^+$	$P$
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

  




# 再谈有限状态机

代码实现:

```
module pulse_FSM (Clock, Resetn, i_pulse, o_pulse);  
    input Clock, Resetn, i_pulse;  
    output reg o_pulse;  
    reg cs, ns; // present and next state variable  
    reg [1:0] pulse_reg;  
    parameter S0 = 0, S1 = 1;
```

```
always @(posedge Clock)  
begin  
    pulse_reg[1] <= pulse_reg[0];  
    pulse_reg[0] <= i_pulse;  
    if (Resetn == 1'b0) // synchronous clear  
        cs <= S0;  
    else  
        cs <= ns;  
end
```

```
always @(cs, pulse_reg[1])  
begin: state_table  
    case (cs)  
        S0: if (pulse_reg[1]) begin  
                ns = S1;  
                o_pulse = 1'b1 end  
            else begin  
                ns = S0;  
                o_pulse = 1'b0; end/  
        S1: if (pulse_reg[1]) begin  
                ns = S1;  
                o_pulse = 1'b0 end  
            else begin  
                ns = S0;  
                o_pulse = 1'b0;  
            default: ns = 2'bxx;  
        endcase  
    end // state_table  
endmodule
```

 


# 再谈有限状态机


## \*Moore Vs Mealy

- ☞ Moore:  $\text{outputs} = f$  (只当前状态)
- ☞ Mealy:  $\text{outputs} = f$  (当前状态, 当前输入)
- ☞ Mealy状态机的输出比Moore快一个周期
- ☞ Mealy状态机比Moore设计复杂, 但可用较少的状态实现同样的功能。

Moore: delayed assertion of P

 

Mealy: immediate assertion of P

 



# 小结

## ※阻塞赋值与非阻塞赋值

- ☞ Always块中阻塞赋值用于组合逻辑;
- ☞ Always块中非阻塞赋值用于时序逻辑;

## ※同步设计及异域时钟的处理

- ☞ 电路使用同步时钟
- ☞ 异域时钟进入先打两拍

## ※有限状态机

- ☞ 多用其输出作为电路的控制信号





# 块 思 雍





# 计算最大公约数

```
int GCD( int inA, int inB)
{
    int done = 0;
    int A = inA;
    int B = inB;
    while ( !done )
    {
        if ( A < B )
        {
            swap = A;
            A = B;
            B = swap;
        }
        else if ( B != 0 )
            A = A - B;
        else
            done = 1;
    }
    return A;
}
```

GCD in C







# 计算最大公约数

```
module gcdGCDUnit_behav#( parameter W = 16 )
( input  [W-1:0] inA, inB,
  output [W-1:0] out );
  reg [W-1:0] A, B, out, swap;
  integer done;
  always @(*)
  begin
    done = 0; A = inA; B = inB;
    while ( !done )
    begin
      if ( A < B )
        swap = A;
        A = B; B = swap;
      else if ( B != 0 )
        A = A - B;
      else
        done = 1;
    end
    out = A; end endmodule
```


用行为级verilog描述GCD





# 电路设计第一步

0、画出方框图外接口：

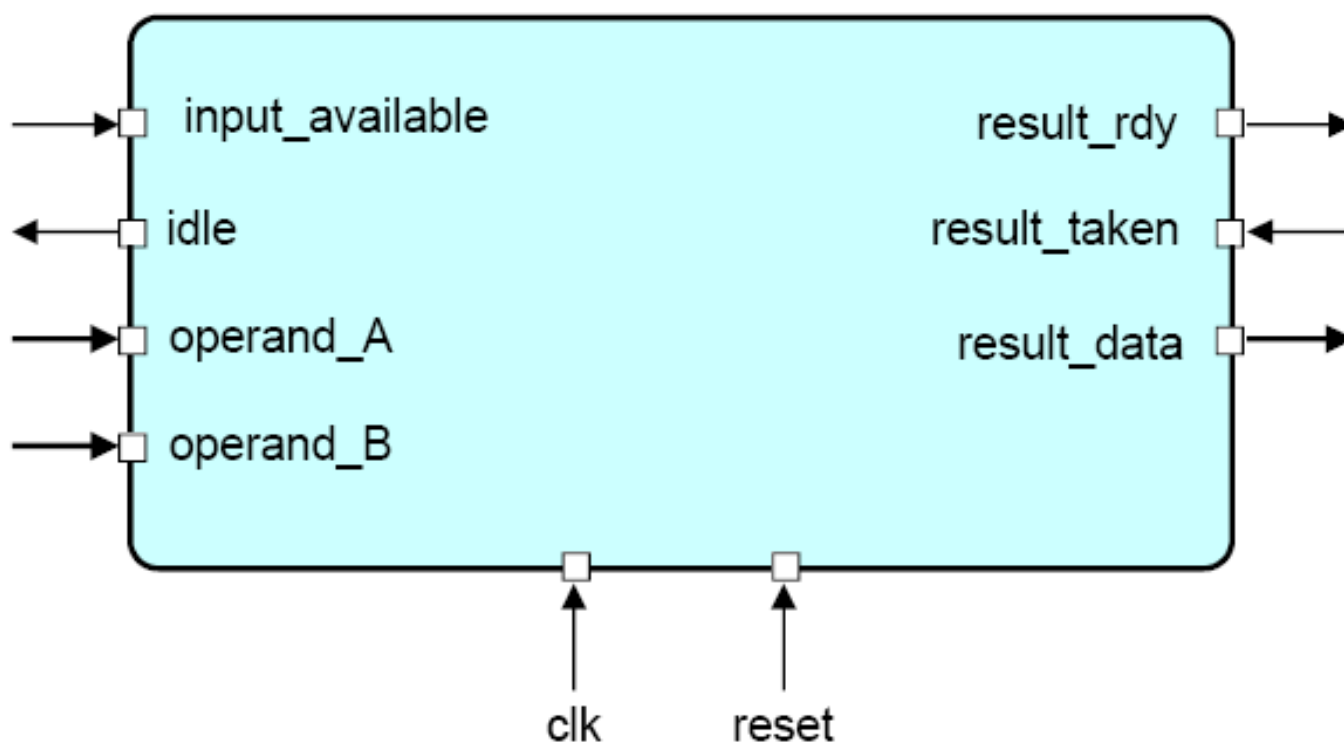



```
module gcdGCDUnit_behav#( parameter W = 16 )
( input  [W-1:0] inA, inB,
  output [W-1:0] out );
reg [W-1:0] A, B, out, swap;
integer done;
always @(*)
begin
  done = 0; A = inA; B = inB;
  while ( !done )
  begin
    if ( A < B )
      swap = A;
      A = B; B = swap;
    else if ( B != 0 )
      A = A - B;
    else
      done = 1;
  end
  out = A; end endmodule
```

What does the RTL  
implementation need?

← State

← Less-Than Comparator


← Equal Comparator

← Subtractor



# 明晰功能，画出方框图内电路

## 1、画出方框图内功能电路：

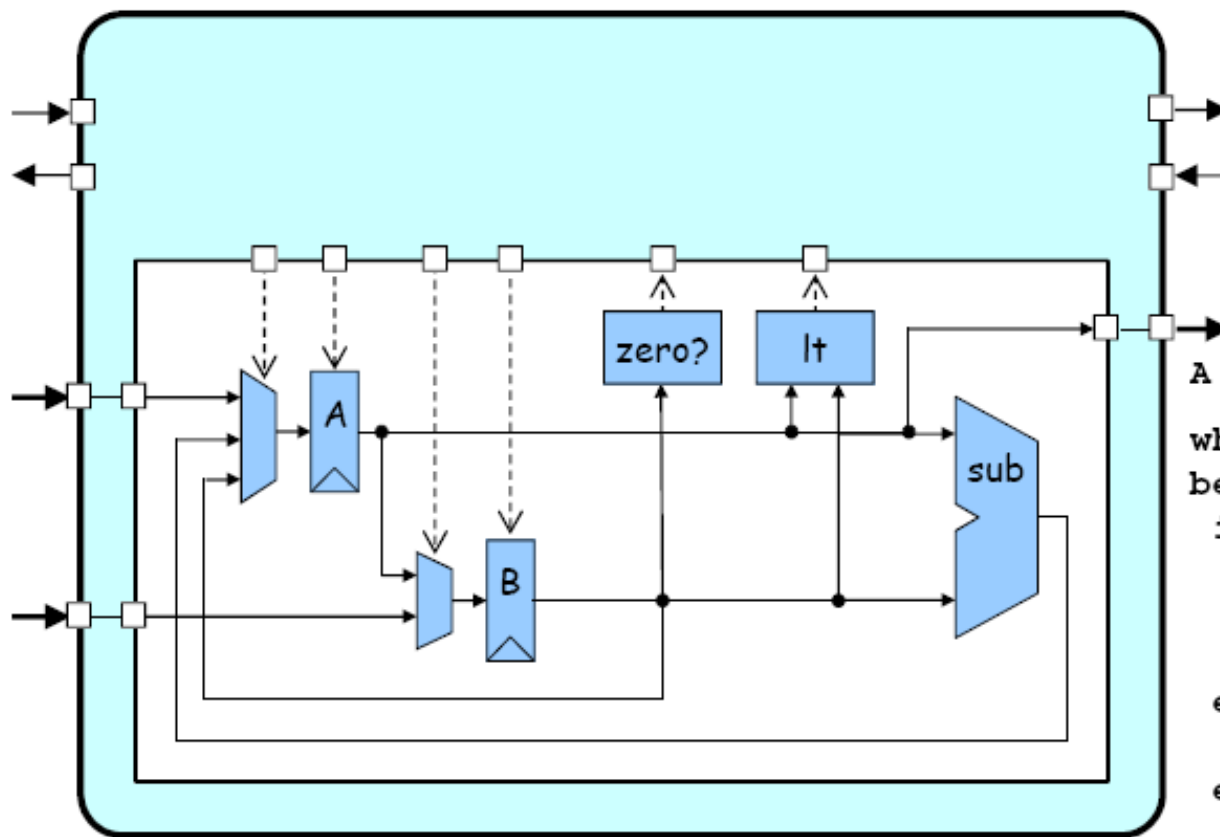


```
A = inA; B = inB;  
while ( !done )  
begin  
  if ( A < B )  
    swap = A;  
    A = B;  
    B = swap;  
  else if ( B != 0 )  
    A = A - B;  
  else  
    done = 1;  
End  
Y = A;
```

确定使用哪个模块，布局布线



清华大学

## 2、画出方框图内控制电路：

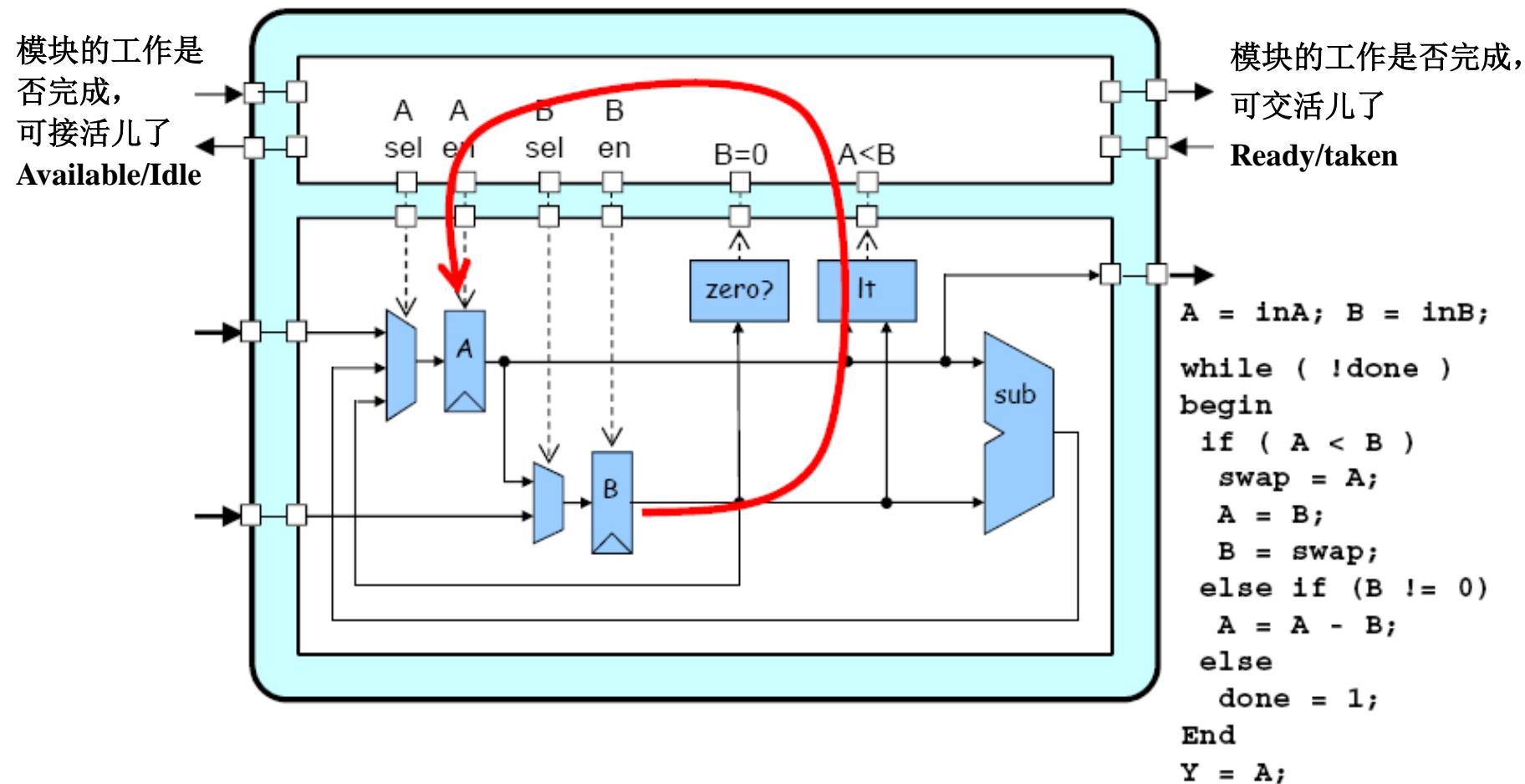



# 功能电路的实现

```
module gcdGCDUnitDpath_sstr#( parameter W = 16 )
```

```
( input      clk,
```

```
// Data signals
```

```
input  [W-1:0] operand_A,
```

```
input  [W-1:0] operand_B,
```

```
output [W-1:0] result_data,
```

```
// Control signals (ctrl->dpath)
```

```
input      A_en,
```

```
input      B_en,
```

```
input  [1:0] A_sel,
```


```
input      B_sel,
```

```
// Control signals (dpath->ctrl)
```

```
output      B_zero,
```

```
output      A_lt_B
```

```
);
```

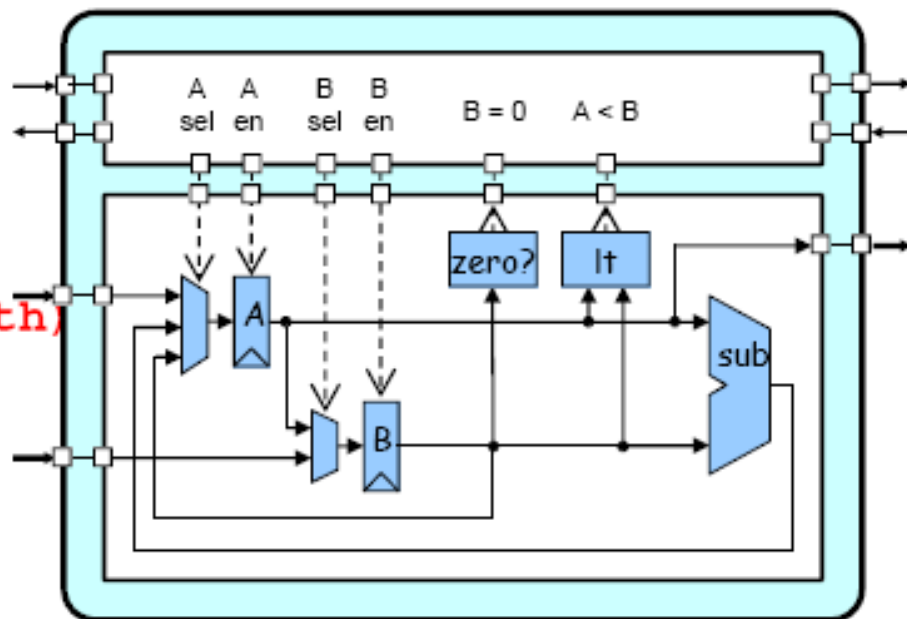



# 功能电路的实现

```

wire [W-1:0] B;
wire [W-1:0] sub_out;
wire [W-1:0] A_out;

```

```

vcMux3#(W) A_mux
( .in0 (operand_A),
  .in1 (B),
  .in2 (sub_out),
  .sel (A_sel),
  .out (A_out) );

```

```


wire [W-1:0] A;

```

```

vcEDFF_pf#(W) A_pf
( .clk (clk),
  .en_p (A_en),
  .d_p (A_out),
  .q_np (A) );

```

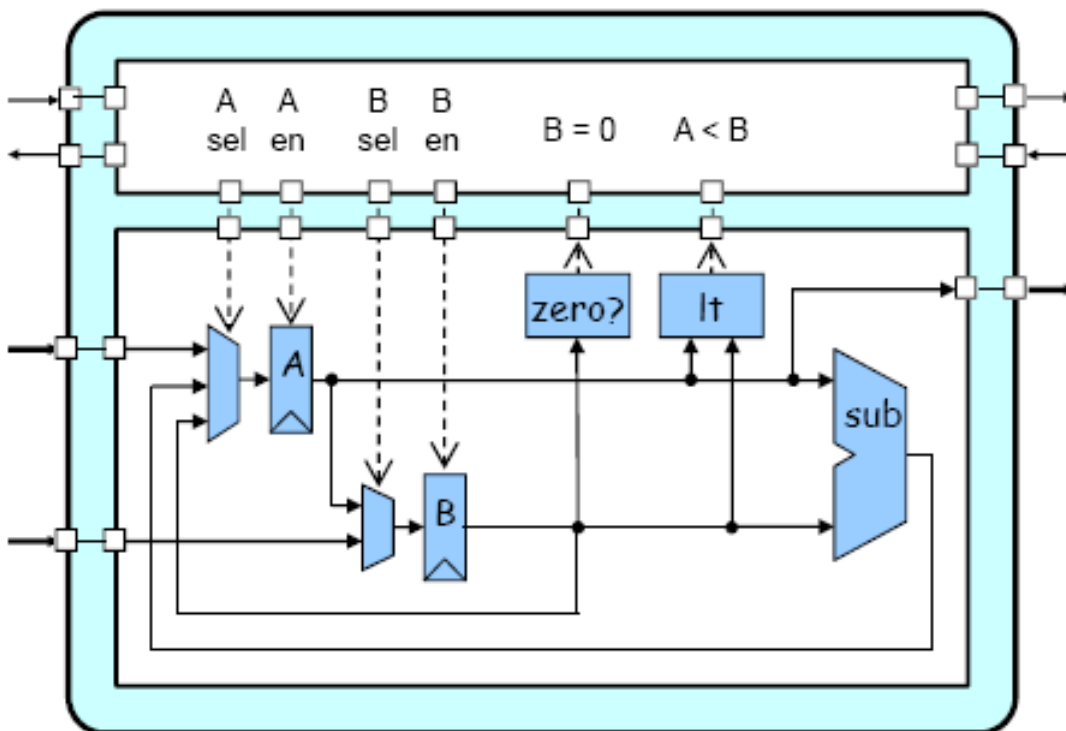





# 功能电路的实现

```
wire [W-1:0] B;  
wire [W-1:0] sub_out;  
wire [W-1:0] A_out;
```

```
vcMux3#(W) A_mux  
( .in0 (operand_A),  
  .in1 (B),  
  .in2 (sub_out),  
  .sel (A_sel),  
  .out (A_out) );
```

```
wire [W-1:0] A;  
vcEDFF_pf#(W) A_pf  
( .clk (clk),  
  .en_p (A_en),  
  .d_p (A_out),  
  .q_np (A) );
```

```
wire [W-1:0] B_out;  
vcMux2#(W) B_mux  
( .in0 (operand_B),  
  .in1 (A),  
  .sel (B_sel),  
  .out (B_out) );
```

```
vcEDFF_pf#(W) B_pf  
( .clk (clk),  
  .en_p (B_en),  
  .d_p (B_out),  
  .q_np (B) );
```

```
assign B_zero = (B==0);  
assign A_lt_B = (A < B);  
assign sub_out = A - B;  
assign result_data = A;
```

需要存储的重要数据，实例化FF，  
使数据在enable信号到来时  
更新FF输出


使用持续赋值语句，描述实时变  
化的组合电路







# 控制电路的实现

 

等待新的操作数

交换 相减 操作

( B = 0 )

等待结果被取走



# GCD的控制单元

```
localparam WAIT = 2'd0;  
localparam CALC = 2'd1;  
localparam DONE = 2'd2;
```

用Localparam  
定义了三个状态

```
reg [1:0] state_next;  
wire [1:0] state;
```

```
vcRDFF_pf#(2,WAIT)  
state_pf  
( .clk      (clk),  
  .reset_p  (reset),  
  .d_p      (state_next),  
  .q_np     (state) );
```

存储当前状态的FF实现





# GCD的控制单元


```
reg [6:0] cs;
always @(*)
begin
    //Default control signals
    A_sel      = A_SEL_X;
    A_en       = 1'b0;
    B_sel      = B_SEL_X;
    B_en       = 1'b0;
    Idle       = 1'b0;
    result_rdy = 1'b0;
    case ( state )
        WAIT :
            ...
        CALC :
            ...
        DONE :
            ...
    endcase
end
```

```
WAIT: begin
    A_sel      = A_SEL_IN;
    A_en       = 1'b1;
    B_sel      = B_SEL_IN;
    B_en       = 1'b1;
    Idle       = 1'b1;
end
CALC: if ( A_lt_B )
    A_sel = A_SEL_B;
    A_en  = 1'b1;
    B_sel = B_SEL_A;
    B_en  = 1'b1;
else if ( !B_zero )
    A_sel = A_SEL_SUB;
    A_en  = 1'b1;
end
DONE: result_rdy = 1'b1;
```
 
# GCD的控制单元

```
always @(*)
begin
    // Default is to stay in the same state
    state_next = state;

    case ( state )
        WAIT :
            if ( input_available )
                state_next = CALC;
        CALC :
            if ( B_zero )
                state_next = DONE;
        DONE :
            if ( result_taken )
                state_next = WAIT;
    endcase
end
```




状态跳变






# GCD模块的测试

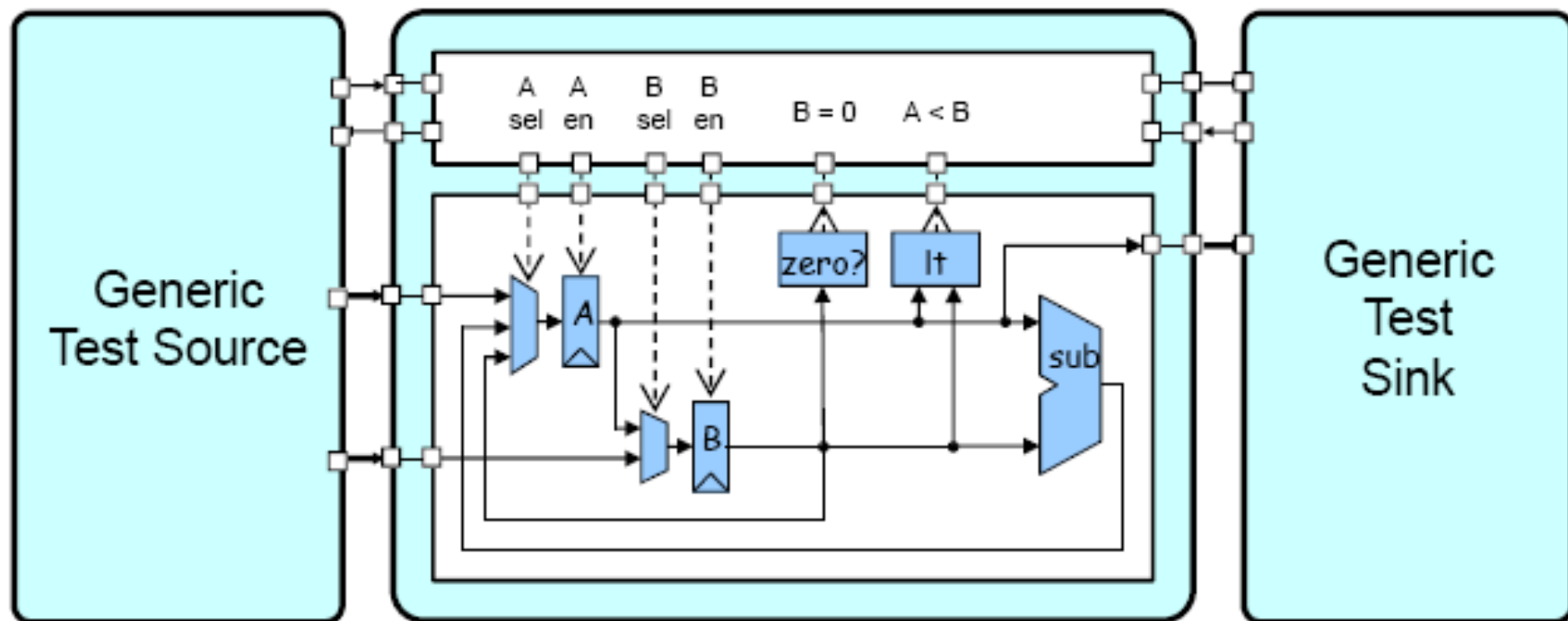

# GCD模块的测试

 



# 代码规范





# 代码规范

[NC-1-R]

A file must contain only one module

- Simplifies source code management

[NC-2-R]

File name has to be identical to module name

- `<module_name>.v`  
`../counter.v`

```
module counter (  
    clk,  
    a_reset_l,  
    inc_h,  
    count  
);  
...
```



# 代码规范

[NC-3-R]

Only [A-Z,a-z,0-9,\_] are allowed for identifier names

[NC-4-R]

Use lower case for port, signal, module and instance names

- Verilog is case sensitiv!

```
module counter(  
    clk,  
    ...  
);  
  
    input  clk;  
    output [3:0] count;  
  
    reg    [3:0] count;  
    ...
```



# 代码规范

[NC-5-R]

Use upper case for parameters

```
parameter DATA_WIDTH = 32;  
parameter ADDR_WIDTH = 8;
```

[NC-6-G]

Instance name should include module name

- Single module instantiation

```
counter counter_1( ... );
```

- Multiple module instantiations

```
counter counter_10( ... );  
counter counter_11( ... );  
counter counter_12( ... );
```



# 代码规范

[NC-7-R]

Use named association port map

```
counter counter_1(  
    clk,  
    a_reset_1,  
    inc_h,  
    count  
);
```

```
counter counter_1(  
    .clk(clk),  
    .a_reset_1(a_reset_1),  
    .inc_h(inc_h),  
    .count(count)  
);
```

[NC-8-G]

Use consistent signal names

```
counter counter_1(  
    .clk(clk2),  
    .a_reset_1(reset),  
    .inc_h(en),  
    .count(data)  
);
```



# 代码规范

[NC-9-G]

Use suffices to differentiate active low/high signals

- `_l` for active low and `_h` for active high

[NC-10-R]

Define only one port per line and use comments

```
...  
input  clk;           //system clock  
input  a_reset_l;    //asynchronous reset, activ low  
...
```

[NC-11-G]

Port order has to be all inputs, inouts, outputs





# 代码规范

[NC-12-G]

Use consistent ordering of bus bits

- Recommended order: MSB to LSB

```
wire [63:0] bus;  
reg  [15:0] data;  
reg  [7:0] addr;
```

[NC-13-R]

Explicitly define bit width for static signal assignments




# 代码规范

[NC-14-R]

Avoid operand size mismatch

- Automatic type cast by zero-extention! Do you really want this?
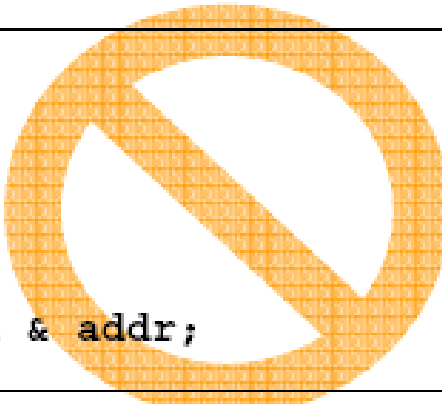
```
wire [63:0] bus;  
reg [15:0] data;  
reg [7:0] addr;  
  
assign bus = data & addr;
```



```
wire [63:0] bus;  
reg [15:0] data;  
reg [7:0] addr;  
  
assign bus = {48'b0, data} & {48'b0, 8'b1, addr};
```





# 代码规范


[SIM-1-R]

Use non-blocking assignments for sequential always blocks

- Verilog race conditions! Order of block execution not defined


```
always @(posedge clk)
begin
    data0 <= data_in;
end

 always @(posedge clk)
begin
    data_out <= data0;
end
```



```
always @(posedge clk)
begin
    data0 = data_in;
end

 always @(posedge clk)
begin
    data_out = data0;
end
```





# 代码规范

[SIM-2-R]

Use blocking assignments for combinational always blocks

- Using of non-blocking assignments for description of combinational logic requires more simulator memory and an extended sensitivity list could be necessary

```
always @(a or b or c)
begin
    d = a & b;
    e = d | c;
end
```

```
always @(a or b or c or d)
begin
    d <= a & b;
    e <= d | c;
end
```

[SIM-3-R]

Don't mix blocking/non-blocking assignments in one always block

- Don't write compact verilog code at the expense of readability
- Clear separation of combinational and sequential logic avoids verilog race conditions and simulation-synthesis mismatch





# 代码规范

[SIM-4-R]

Don't make assignments to a signal from different always blocks

- Order of block execution is not defined, potential Verilog race condition/simulation-synthesis mismatch

```
always @(a or b)
begin
    e = a | b;
end
```

```
always @(c or d)
begin
    e = c & d;
end
```



# 代码规范

[SIM-5-R]

Sensitivity list of combinational always block has to be complete

- Incomplete sensitivity list could lead to simulation-synthesis mismatch

```
always @(a)
begin
    c = a | b;
end
```




[SIM-6-R]

Avoid unnecessary signals in sensitivity list

- Additional signals could result in a reduced simulation performance

```
always @(a or b or x)
begin
    c = a | b;
end
```

 

# 代码规范


[SIM-7-R]

Flip-Flops have to have either a set or a reset

- To transfer the design to a defined state for simulation

 
## *Asynchronous reset/set*

```
always @(posedge clk or negedge a_reset_1)
begin
    if (a_reset_1 == 1'b0) begin
        a <= 1'b0;
        b <= 1'b1;
    end
    else begin
        ...
    end
end
```


 
## *Synchronous reset/set*

```
always @(posedge clk)
begin
    if (syn_reset_1 == 1'b0) begin
        a <= 1'b0;
        b <= 1'b1;
    end
    else begin
        ...
    end
end
```



# 代码规范

[SYN-1-R]

Incomplete case statements have to have default case

- No unexpected latches are inferred

```
always @(condition)
begin
  case (condition)
    2'b00   : ...
    2'b01   : ...
    2'b10   : ...
    default : ...
  end case
end
```








# 代码规范

[SYN-2-R]

Combinational feedback loops are forbidden

 - Combinational feedback loop will cause problems during timing analysis






# 代码规范

[SYN-3-G]

All module outputs should be registered

 - Simplifies synthesis constraints (*set\_input\_delay*, *set\_output\_delay*)




# 代码规范

[DFT-1-R]

Avoid internally generated set/reset signals

 - Full set/reset control is required for scan operation



[DFT-2-R]

Avoid internally generated clocks

- Full clock control is required for scan operation





# 知识点小结



- ✱ 阻塞赋值与非阻塞赋值
- ✱ 同步设计及异域时钟的处理
- ✱ 再谈有限状态机
- ✱ 块思维
- ✱ 代码规范

