



计算机科学基础 C



北京¹大学



简单 CPU 设计



清华大学²



设计简单CPU

CPU位宽：16位

指令格式声明：

III XXX YYY,

III 表示指令，**XXX** 表示Rx寄存器，**YYY** 表示Ry寄存器，**Miv**指令后跟随输入数据是16位立即数D。

指令编码表：

000:	mv	Rx,Ry	// Rx <- [Ry]
001:	mvi	Rx,#D	// Rx <- D
010:	add	Rx, Ry	// Rx <- [Rx] + [Ry]
011:	sub	Rx, Ry	// Rx <- [Rx] - [Ry]





怎么做？

块思维思想：运筹帷幄，布局规划，驾驭你的模块！

块思维方法：

- 1、分析CUP外有哪些port？
- 2、思考CPU内有哪些block？


port:

DIN, BusWires, Resetn, Clock, Run, Done

block:

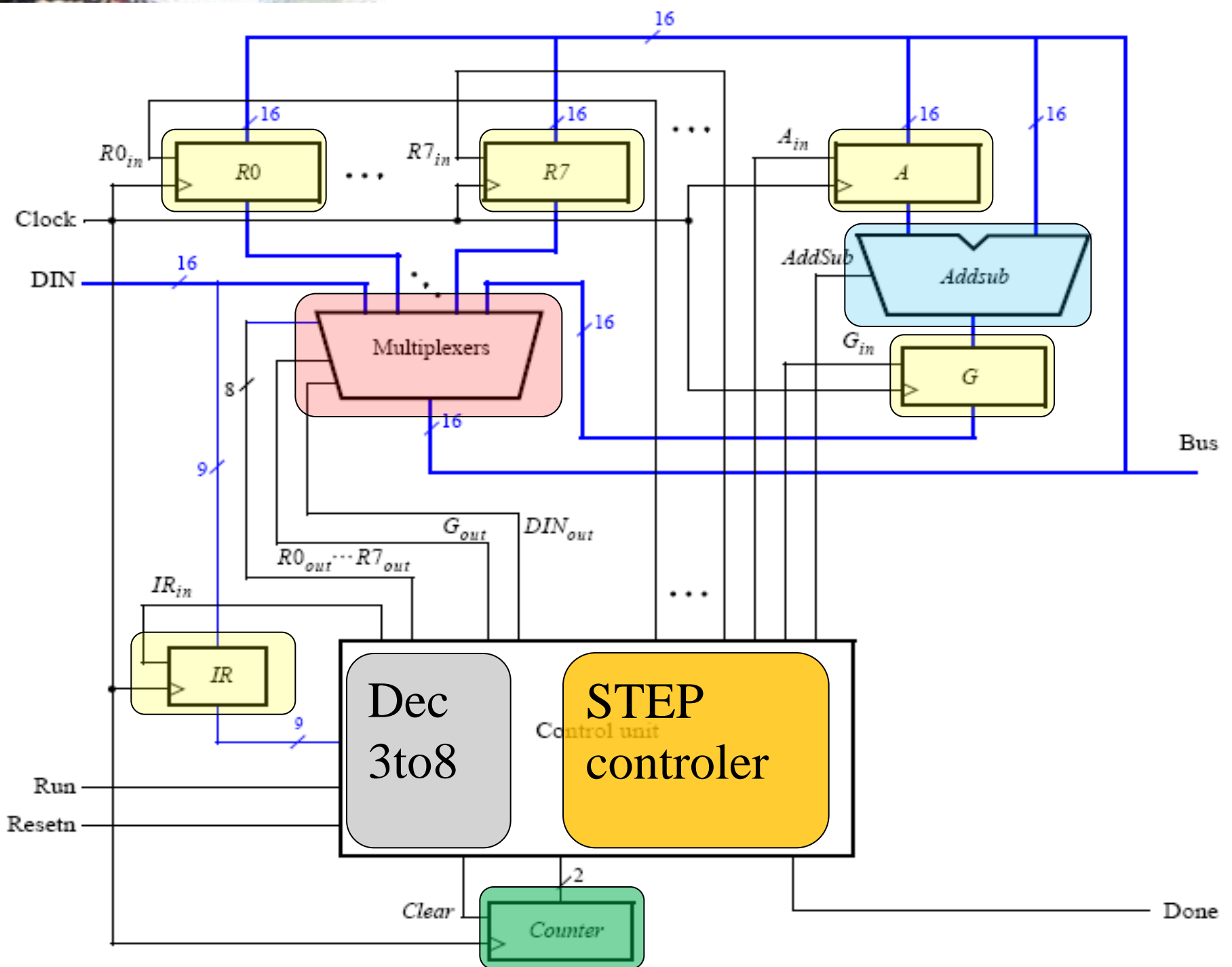
alu(addsub), controler, regn, mux, upcount, dec3to8





控制时序

指令 \ 时间				
	T0 →	T1 →	T2 →	T3 →
(mv):I ₀	IR _{in}	RY _{out} , RX _{in} , Done	—	—
(mvi):I ₁	IR _{in}	DIN _{out} , RX _{in} , Done	—	—
(add):I ₂	IR _{in}	RX _{out} , A _{in}	RY _{out} , G _{in}	G _{out} , RX _{in} , Done
(sub):I ₃	IR _{in}	RX _{out} , A _{in}	RY _{out} , G _{in} , Addsub	G _{out} , RX _{in} , Done

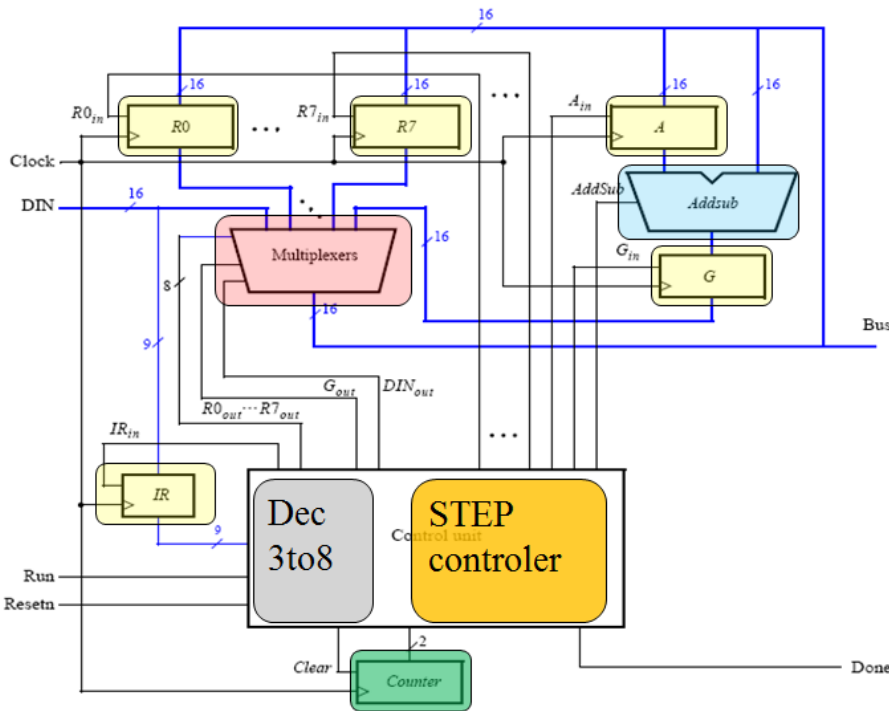

Rout表示把某个寄存器中的数据
放出到汇流台

Rin表示把汇流台中的数据
放入指定的R寄存器



清华大学



指令 \ 时间	<div>用组合电路准备 clk触发前瞬间更新</div> <div>用组合电路准备 clk触发前瞬间更新</div> <div>用组合电路准备 clk触发前瞬间更新</div> <div>用组合电路准备 clk触发前瞬间更新</div>			
	T0 →	T1 →	T2 →	T3 →
(mv):I ₀	IR _{in}	RY _{out} , RX _{in} , Done	—	—
(mvi):I ₁	IR _{in}	DIN _{out} , RX _{in} , Done	—	—
(add):I ₂	IR _{in}	RX _{out} , A _{in}	RY _{out} , G _{in}	G _{out} , RX _{in} , Done
(sub):I ₃	IR _{in}	RX _{out} , A _{in}	RY _{out} , G _{in} , Addsub	G _{out} , RX _{in} , Done

Mvi R3,5 001 011 (SW15-SW0)

.....101

clk1个T0

clk1个T1

Mvi R7,9 001 111

.....1001

clk1个T0

clk1个T1

Add R3,R7 010 011 111...

clk3个T0 T1 T2 出


现到总线，1个clkT3进入R3



北京大學


AddSub

```
1 //Name: AddSub
2 //Function:
3 //      AddSub = 0 Add
4 //      AddSub = 1 Sub
5 //Author: caojian
6
7 module addsub(AddSub, A, BusWires, Sum);
8   input AddSub;
9   input[15:0] A, BusWires;
10  output[15:0] Sum;
11  reg[15:0] Sum;
12
13  always@(AddSub or A or BusWires)
14  begin
15      if(!AddSub)
16          Sum = A + BusWires;
17      else
18          Sum = A - BusWires;
19  end
20
21 endmodule
22
```

 

busmux

```
1 //Name: busmux
2 //Function:
3 //      select which reg push to bus
4 //Author: caojian
5 module busmux(Rout, Gout, DINout, R0, R1, R2, R3, R4, R5, R6, R7, G, DIN, BusWires);
6 input[7:0] Rout;
7 input Gout, DINout;
8 input[15:0] R0, R1, R2, R3, R4, R5, R6, R7, G, DIN;
9 output[15:0] BusWires;
10 reg[15:0] BusWires;
11 wire[9:0] Sel;
12 assign Sel = {Rout, Gout, DINout};
13 always@(*)
14 begin
15     if(Sel == 10'b1000000000)
16         BusWires = R0;
17     else if(Sel == 10'b0100000000)
18         BusWires = R1;
19     else if(Sel == 10'b0010000000)
20         BusWires = R2;
21     else if(Sel == 10'b0001000000)
22         BusWires = R3;
23     else if(Sel == 10'b0000100000)
24         BusWires = R4;
25     else if(Sel == 10'b0000010000)
26         BusWires = R5;
27     else if(Sel == 10'b0000001000)
28         BusWires = R6;
29     else if(Sel == 10'b0000000100)
30         BusWires = R7;
31     else if(Sel == 10'b0000000010)
32         BusWires = G;
33     else BusWires = DIN;
34 end
```

 

select which reg push to bus


dec3to8

```
1 //File name: dec3to8
2 //Function: dec 3 to 8
3 //Author: Zhang Lei
4
5 module dec3to8 (W, En, Y);
6
7     input [2:0] W;
8     input  En;
9     output[7:0] Y;
10    reg  [7:0] Y;
11
12
13    always @ (W or En)
14    begin
15        if(En == 1)
16            case(W)
17                3'b000: Y = 8'b10000000;
18                3'b001: Y = 8'b01000000;
19                3'b010: Y = 8'b00100000;
20                3'b011: Y = 8'b00010000;
21                3'b100: Y = 8'b00001000;
22                3'b101: Y = 8'b00000100;
23                3'b110: Y = 8'b00000010;
24                3'b111: Y = 8'b00000001;
25            endcase
26        else
27            Y = 8'b00000000;
28        end
29
30    endmodule
```




regn

 
```
1 //File name:regn.v
2 //Function:Register,posedge clock active.
3 //Author:Eric Liu
4 module regn(R,Rin,Clock,Q) ;
5     parameter n = 16;
6     input[n-1:0] R;
7     input Rin,Clock;
8     output[n-1:0] Q;
9     reg [n-1:0] Q;
10
11     always @(posedge Clock)
12         if(Rin)
13             Q <= R;
14 endmodule
```



upcounte
 
```
1 //File: upcount.v
2 //Function: a counter for the instructions
3 //Author: Caojian
4 module upcount(Clear,Clock,Q);
5     input Clear,Clock;
6     output [1:0] Q;
7     reg [1:0] Q;
8
9     always @(posedge Clock)
10         if (Clear)
11             Q <= 2'b0;
12         else
13             Q <= Q+1'b1;
14 endmodule
```



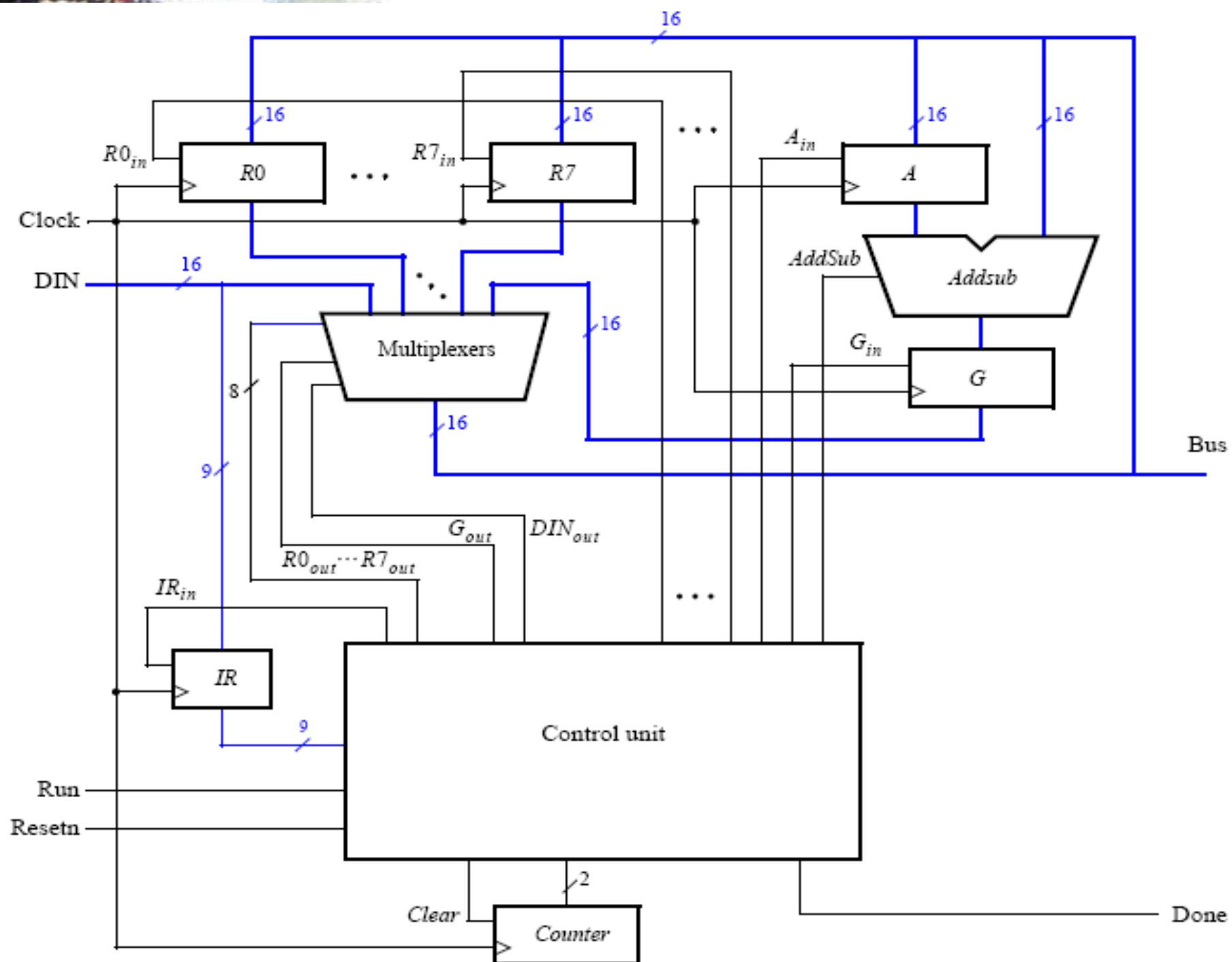



CPU效果展示

用SW15-SW0驱动DIN;

用SW17作为Run;

KEY0作为Resetcn;

KEY1作为Clock

总线接到LEDR15-LEDR0

Done接到LEDR17





完成prob.v的编写，上板调试。



作业：

完成简单的CPU设计

邮件标题：CPU1_学号_姓名

内容：附件：proc.v

